

Comparing Circuits Activity

| | |
|--|--|
| <p>My observations about series circuits:</p> <p>*Try to include a labeled drawing or image of the series circuit you created.</p> | |
| <p>My observations about parallel circuits:</p> <p>*Try to include a labeled drawing or image of the parallel circuit you created.</p> | |
| <p>Similarities between series and parallel circuits:</p> | |

Comparing Circuits Activity

| | |
|--|--|
| Differences between series and parallel circuits: | |
| What are some advantages and disadvantages of series and parallel circuits? | |
| What is a real-life situation where using one type of circuit might be more beneficial than using the other? Explain your reasoning. | |

Comparing Circuits Activity

| | |
|---|--|
| <p>Why is a switch beneficial to have in a circuit?</p> | |
| <p>Lingering questions that I still have:</p> | |
| <p>Additional notes or conclusions that I can make about series and parallel circuits (optional):</p> | |